
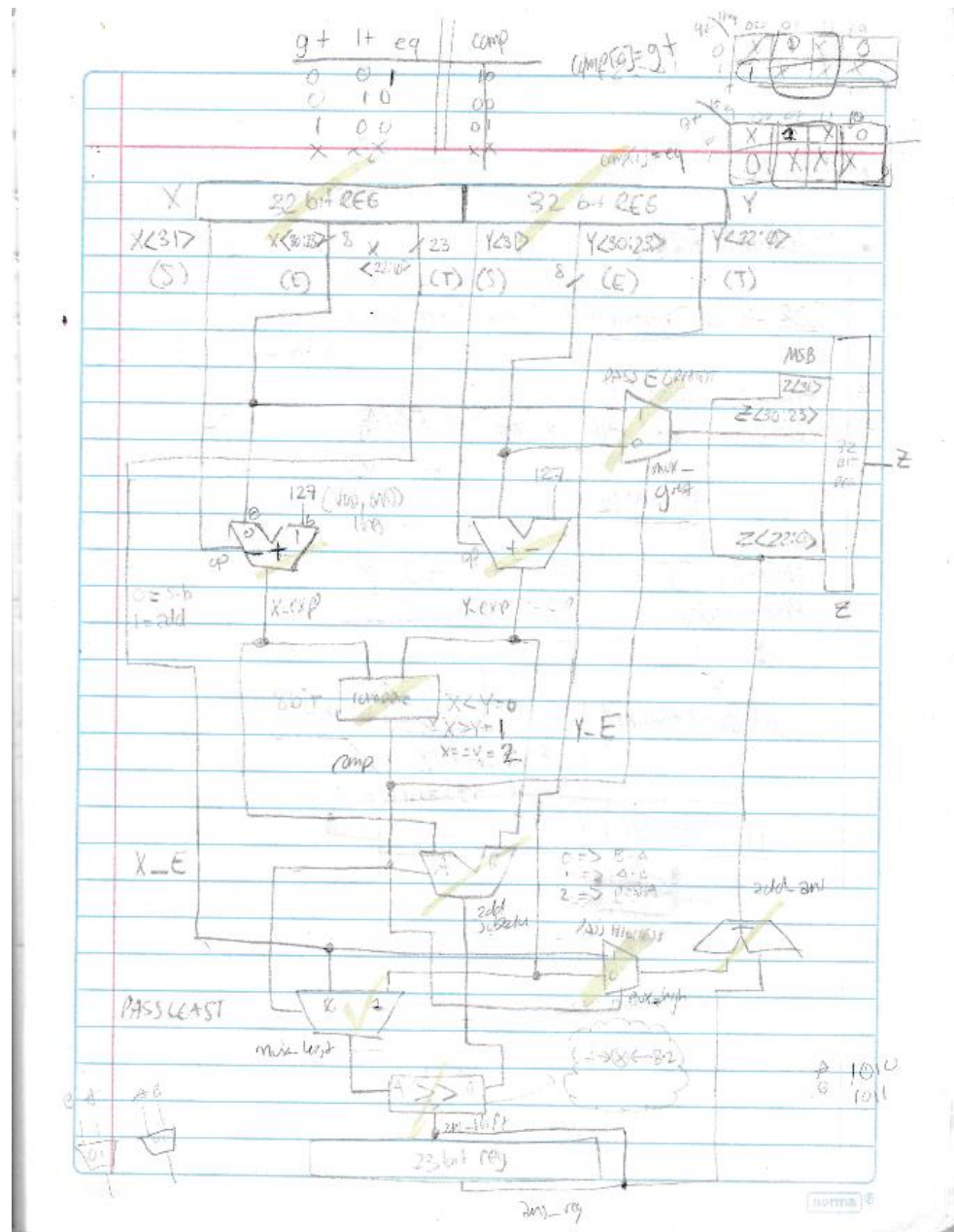


ARCHITECTURE DESIGN FROM SCRATCH

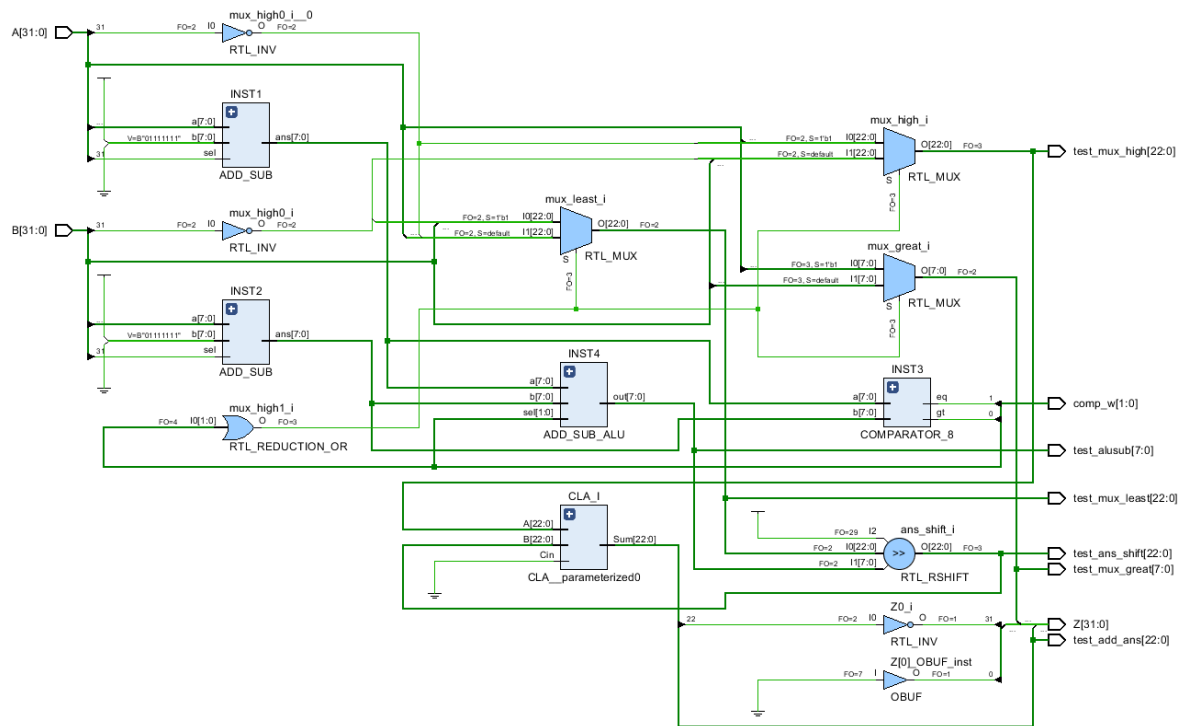

ELABORATED DESIGN



SIMULATION

> a[31:0]	420f0000	420f0000
> b[31:0]	41a40000	41a40000
> z[31:0]	42610000	42610000


RTL COMPILER

```

Done mapping IEEE754
Synthesis succeeded.
Warning : Possible timing problems have been detected in this design. [TIM-11]
         : The design is 'IEEE754'.
         : Use 'report timing -lint' for more information.
rc:/> write_sdc > IEEE754.sdc
Finished SDC export (command execution time mm:ss (real) = 00:00).
rc:/>

```

IC LAYOUT

 

TIMING REPORT

DRVs	Real		Total
	Nr nets(terms)	Worst Vio	Nr nets(terms)
max_cap	0 (0)	0.000	0 (0)
max_tran	0 (0)	0.000	0 (0)
max_fanout	0 (0)	0	0 (0)
max_length	0 (0)	0	0 (0)

Density: 52.979%

Routing **Overflow**: 0.00% H and 0.00% V

Reported timing to dir ./timingReports

Total CPU time: 0.29 sec

Total Real time: 10.0 sec

Total Memory Usage: 804.503906 Mbytes

encounter 1> █

POST ROUTE TIMING

DRVs	Real		Total
	Nr nets(terms)	Worst Vio	Nr nets(terms)
max_cap	0 (0)	0.000	0 (0)
max_tran	0 (0)	0.000	0 (0)
max_fanout	0 (0)	0	0 (0)
max_length	0 (0)	0	0 (0)

Density: 52.979%

Total number of glitch violations: 0

Reported timing to dir timingReports

Total CPU time: 0.2 sec

Total Real time: 1.0 sec

Total Memory Usage: 864.804688 Mbytes

encounter 1> █

VERIFY GEOMETRY

```
VERIFY GEOMETRY ..... Cells           : 0 Viols.
VERIFY GEOMETRY ..... SameNet          : 0 Viols.
VERIFY GEOMETRY ..... Wiring           : 0 Viols.
VERIFY GEOMETRY ..... Antenna          : 0 Viols.
VERIFY GEOMETRY ..... Sub-Area : 1 complete 0 Viols. 0 Wrngs.
VG: elapsed time: 0.00
Begin Summary ...
Cells           : 0
SameNet         : 0
Wiring          : 0
Antenna         : 0
Short           : 0
Overlap         : 0
End Summary

Verification Complete : 0 Viols. 0 Wrngs.

*****End: VERIFY GEOMETRY*****
*** verify geometry (CPU: 0:00:00.1 MEM: 2.1M)

encounter 1> █
```

VERIFY CONNECTIVITY

```
encounter 1> VERIFY_CONNECTIVITY use new engine.

***** Start: VERIFY CONNECTIVITY *****
Start Time: Fri Nov 8 01:04:53 2019

Design Name: IEEE754
Database Units: 2000
Design Boundary: (0.0000, 0.0000) (155.5300, 141.0400)
Error Limit = 1000; Warning Limit = 50
Check all nets

Begin Summary
Found no problems or warnings.
End Summary

End Time: Fri Nov 8 01:04:53 2019
Time Elapsed: 0:00:00.0

***** End: VERIFY CONNECTIVITY *****
Verification Complete : 0 Viols. 0 Wrngs.
(CPU Time: 0:00:00.0 MEM: 0.000M)


encounter 1> █
```

GDS FILE

```
Metal Fills          0
  Via Instances      0
Metal Fill0PCs       0
  Via Instances      0
Text                 0
Blockages            0
Custom Text          0
Custom Box           0

**WARN: (ENC0GDS-1176): There are 6 empty cells. Check encounter.log# for the details.
  It is probably because your mapping file does not contain corresponding rules.
  Use default mapping file(without option -mapFile) to output all information of a cell.
#####Streamout is finished!
encounter 1> █
```

SCHEMATIC VIEWER

 

VERILOG CODE

```
`timescale 1ns / 1ps

module IEEE754(
input  [31:0] A,B,

output [31:0] Z,
output [1:0] comp_w,
output [7:0] test_alusub, test_mux_great,
output [22:0] test_mux_least, test_ans_shift, test_mux_high, test_add_ans
);

wire [7:0] x_exp, y_exp;

ADD_SUB INST1(
.a(A[30:23]),
.b(8'd127),
.sel(A[31]),

.ans(x_exp),
.carry()
);

ADD_SUB INST2(
.a(B[30:23]),
.b(8'd127),
.sel(B[31]),

.ans(y_exp),
.carry()
);

wire gt,lt,eq;
wire [1:0] comp;

COMPARATOR_8 INST3(
.a(x_exp),
.b(y_exp),
```

```

.gt(gt),
.lt(lt),
.eq(eq)
);

assign comp = {eq,gt};
assign comp_w = comp;

wire [7:0] addsubalu;
assign test_alusub = addsubalu;

ADD_SUB_ALU INST4(
.a(x_exp),
.b(y_exp),
.sel(comp),

.out(addsubalu)
);

wire [22:0] mux_least;
wire [22:0] ans_shift;

assign mux_least = comp ? {~B[31], B[22:1]} : {~A[31], A[22:1]};
assign test_mux_least = mux_least;

assign ans_shift = mux_least >> addsubalu;
assign test_ans_shift = ans_shift;

wire [22:0] mux_high;
assign mux_high = comp ? {~A[31], A[22:1]} : {~B[31], B[22:1]};
assign test_mux_high = mux_high;

wire [22:0] add_ans;
assign test_add_ans = add_ans;

CLA #(23) CLA_I(
.A(mux_high),

```



```

.B(ans_shift),
.Cin(1'b0),

.Sum(add_ans),
.Cout()
);

wire [7:0] mux_great;
assign mux_great = comp ? A[30:23] : B[30:23];
assign test_mux_great = mux_great;

assign Z = ({~add_ans[22], mux_great, {add_ans[21:0], 1'b0}});

endmodule

module COMPARATOR_8(
input [7:0] a, b,
output gt,lt,eq

);

wire [1:0] gt_in, lt_in, eq_in;

COMPARATOR_4 COMP_1(
.a(a[7:4]),
.b(b[7:4]),

.gt(gt_in[1]),
.lt(lt_in[1]),
.eq(eq_in[1])
);

COMPARATOR_4 COMP_2(
.a(a[3:0]),
.b(b[3:0]),

.gt(gt_in[0]),

```

```
.lt(lt_in[0]),  
.eq(eq_in[0])  
);
```

```
GLUE GLUE_1(  
.gt_in(gt_in),  
.lt_in(lt_in),  
.eq_in(eq_in),
```

```
.gt_out(gt),  
.lt_out(lt),  
.eq_out(eq)  
);
```

```
endmodule
```

```
module COMPARATOR_4(  
    input [3:0] a, b,  
    output gt,lt,eq  
);
```

```
wire [1:0] gt_in, lt_in, eq_in;
```

```
COMPARATOR HI(  
.a(a[3:2]),  
.b(b[3:2]),  
  
.gt(gt_in[1]),  
.lt(lt_in[1]),  
.eq(eq_in[1])  
);
```

```
COMPARATOR LO(  
.a(a[1:0]),  
.b(b[1:0]),  
  
.gt(gt_in[0]),
```

```
.lt(lt_in[0]),  
.eq(eq_in[0])  
);
```

```
GLUE GLUE_I(  
.gt_in(gt_in),  
.lt_in(lt_in),  
.eq_in(eq_in),
```

```
.gt_out(gt),  
.lt_out(lt),  
.eq_out(eq)  
);
```

```
endmodule
```

```
module GLUE (  
    input [1:0] gt_in, lt_in, eq_in,  
    output gt_out, lt_out, eq_out  
);
```

```
    wire [1:0] and_w;
```

```
//lvl 1  
and(and_w[1], eq_in[1], gt_in[0]);  
and(and_w[0], eq_in[1], lt_in[0]);
```

```
//lvl 2  
or(gt_out, gt_in[1], and_w[1]);  
or(lt_out, lt_in[1], and_w[0]);  
and(eq_out, eq_in[1], eq_in[0]);
```

```
endmodule
```

```
module COMPARATOR(  
    input [1:0] a, b,
```

```

output gt, lt, eq
);

assign lt = ~a[1] & b[1] | ~a[1] & ~a[0] & b[0] | ~a[0] & b[1] & b[0];
assign gt = a[1] & ~b[1] | a[0] & ~b[1] & ~b[0] | a[1] & a[0] & ~b[0];
assign eq = ~a[1]&~a[0]&~b[1]&~b[0] | ~a[1] & a[0] & ~b[1] & b[0] | a[1] & a[0] & b[1] & b[0] | a[1] &
~a[0] & b[1] & ~b[0];

endmodule

//Wrapper for Carry-Lookahead-Logic and Partial Full Adders
module CLA #(parameter bits = 8) ( //parameter to specify number of bits for adder
input [bits-1:0] A, B, //augend and addend
input Cin, //first carry in

output [bits-1:0] Sum, //sum output
output Cout //carry out bit

//output [bits-1:0]carries //for testbench
);

wire [bits-1:0]P_in, G_in; //wire bus for propagate and generate bits
wire [bits-1:0]carries; //wire bus for carry bits

assign Cout = carries[bits-1]; //propagate last carry out from msb of carries bus

//create partial full adder instance for the first bit to incorporate Cin
PFA PFA0(
.A(A[0]),
.B(B[0]),
.Cin(Cin),

.P(P_in[0]),
.G(G_in[0]),
.S(Sum[0])

);

```

```

genvar i;
generate //Instantiate N PFA's for bits
    for(i=1; i<bits; i=i+1) begin : PFAS
        PFA PFA_I(
            .A(A[i]),
            .B(B[i]),
            .Cin(carries[i-1]),

            .P(P_in[i]),
            .G(G_in[i]),
            .S(Sum[i])
        );
    end
endgenerate

//Instantiate Carry-Lookahead-Logic block
CLL #(.bits(bits)) CLL_INST(
    .Cin(Cin),
    .P(P_in),
    .G(G_in),

    .Cout(carries)
);

endmodule

////////////////////////////////////
//This module handles the carry outs for each partial full adder
//Acts as a wrapper to individual carry_gen modules
module CLL #(parameter bits = 8) (
    input Cin,
    input [bits-1: 0] P, G,
    output [bits-1: 0] Cout
);

//Create carry generator block for first bit
CARRY_GEN INST0(

```

```

        .G(G[0]),
        .P(P[0]),
        .Cin(Cin),

        .Cout(Cout[0])
    );

    genvar i;
    generate //Create N bits of carry generators
        for(i=1; i < bits; i=i+1) begin : CARRIES
            CARRY_GEN INST_I(
                .G(G[i]),
                .P(P[i]),
                .Cin(Cout[i-1]),

                .Cout(Cout[i])
            );

        end
    endgenerate
endmodule

/////////////////////////////////////////////////////////////////
module ADD_HALF(
    output cout,
    output sum,
    input a,
    input b
);
    xor(sum, a, b);
    and(cout, a, b);
endmodule

/////////////////////////////////////////////////////////////////
//Calculates the propagate, generate, and sum bits
module PFA(
    input A, B, Cin,
    output P, G, S

```

```

);

    assign P = A ^ B;    //xor gate for propagate
    assign G = A & B;    // and gate for generate
    assign S = Cin ^ P; // xor gate for sum

endmodule
////////////////////////////////////
module FULL_ADDER(
    input a,b,cin,
    output cout,sum

);

wire half1_cout, half1_sum, half2_cout;

ADD_HALF HALF1(
.cout(half1_cout),
.sum(half1_sum),
.a(a),
.b(b)
);

ADD_HALF HALF2(
.cout(half2_cout),
.sum(sum),
.a(cin),
.b(half1_sum)
);

//for the carry out of both half adders
or(cout, half2_cout, half1_cout);

endmodule
////////////////////////////////////
//Calculates the carry using generate, propagate, and carry in bits
module CARRY_GEN(

```

```

        input G, P, Cin,
        output Cout
    );

    assign Cout = G | P&Cin; //wire out carry calculation

endmodule

////////////////////////////////////

module ADD_SUB_ALU(
    input [7:0] a,b,
    input [1:0] sel,
    output reg [7:0] out
);

    //0 is B-A
    //1 is A-B
    //2 is pass A

    always@(*) begin
        case(sel)
            2'b00: begin
                out = b-a;
            end
            2'b01: begin
                out = a-b;
            end
            2'b10: begin
                out = a;
            end
            2'b11: begin
                out = out;
            end
        endcase
    end
end

```



```

/*
CLA #(8) CLA_I(
.A(mux_1),
.B(mux_2),
.Cin(1'b0),

.Sum(m_b),
.Cout(carry)
);
*/

endmodule

//if sel ==0 subtract A-B
//if sel ==1 add A+B
module ADD_SUB(
input [7:0] a, b,
input sel,

output [7:0] ans,
output carry

);
wire [7:0] add, sub;
wire [7:0] b_cla;

//(8'h7F)
assign b_cla = sel ? b : (~b + 1);

CLA #(8) CLA_I(
.A(a),
.B(b_cla),
.Cin(1'b0),

.Sum(ans),
.Cout(carry)

```

```
);  
endmodule
```